


2 Stage OTA Simulations

Roll no. **240102111**

Name : **Tanmay Singh**




Non inverting
amplifier with
gain 2

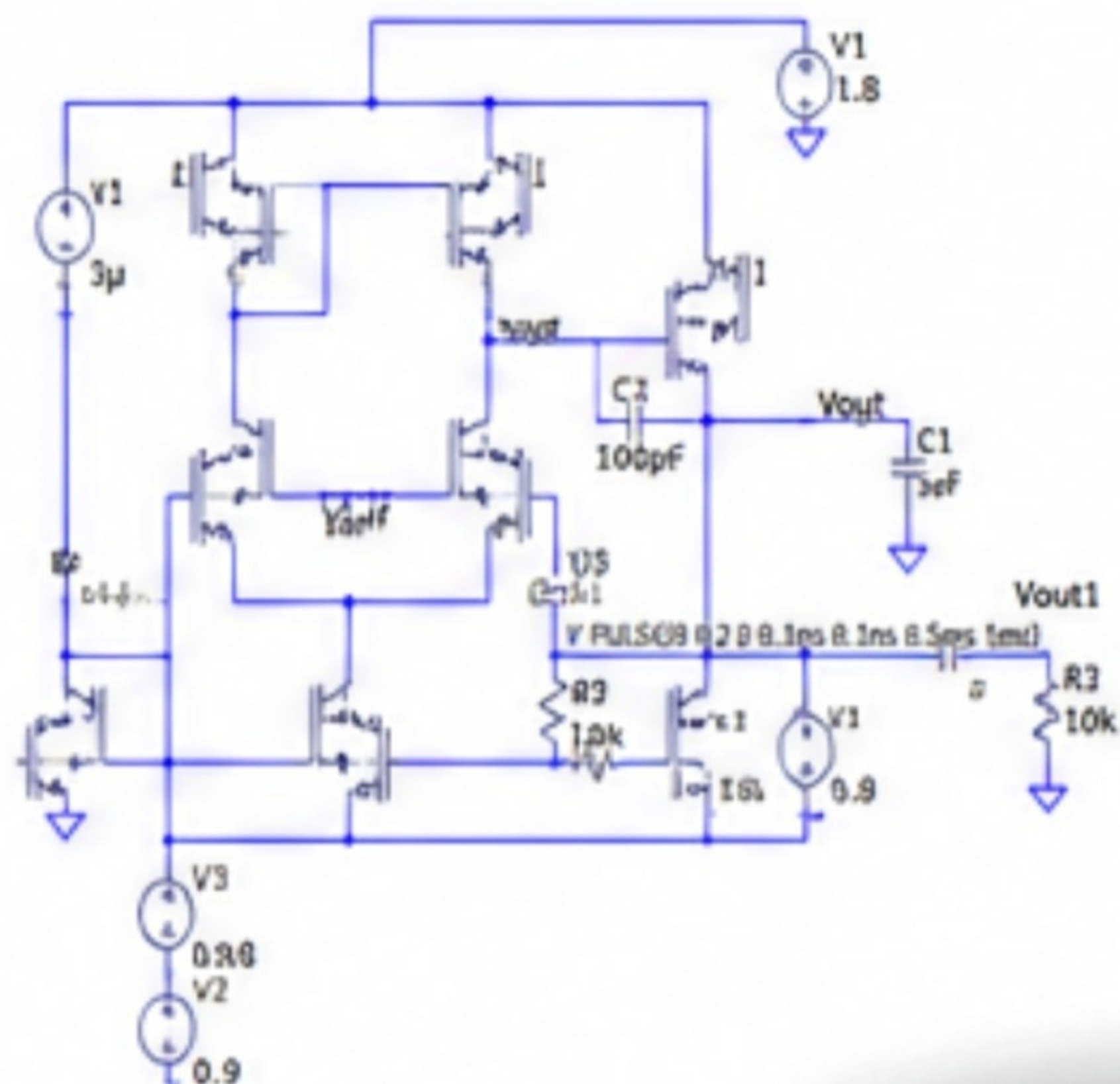


.tran 5ms

Simulation with Input pulse of 0.2V(black) giving output 0.4V(Blue).....at terminal
Vout


LTspice XVII - OTA_TANMAY_final

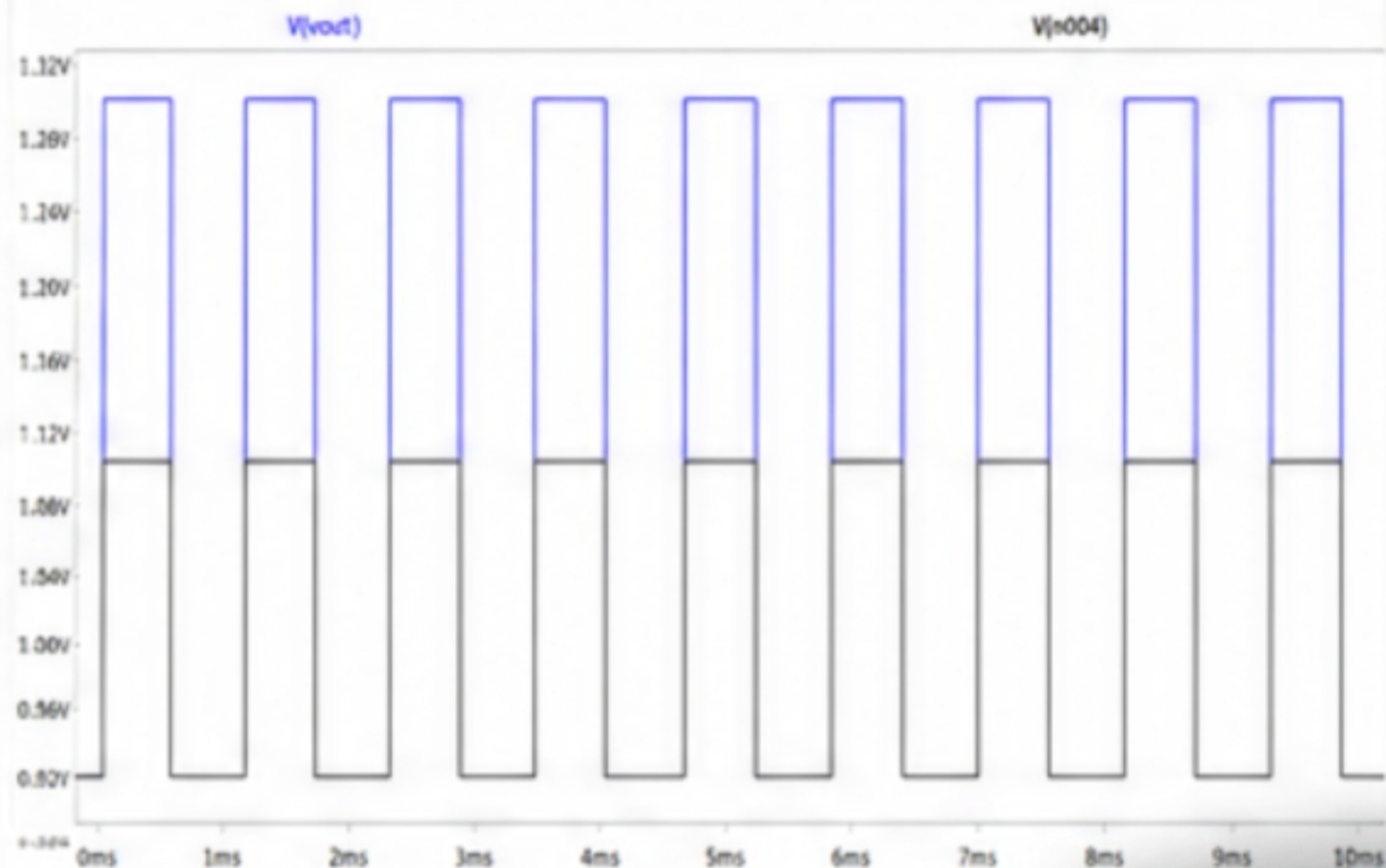

Output taken at terminal Vout1

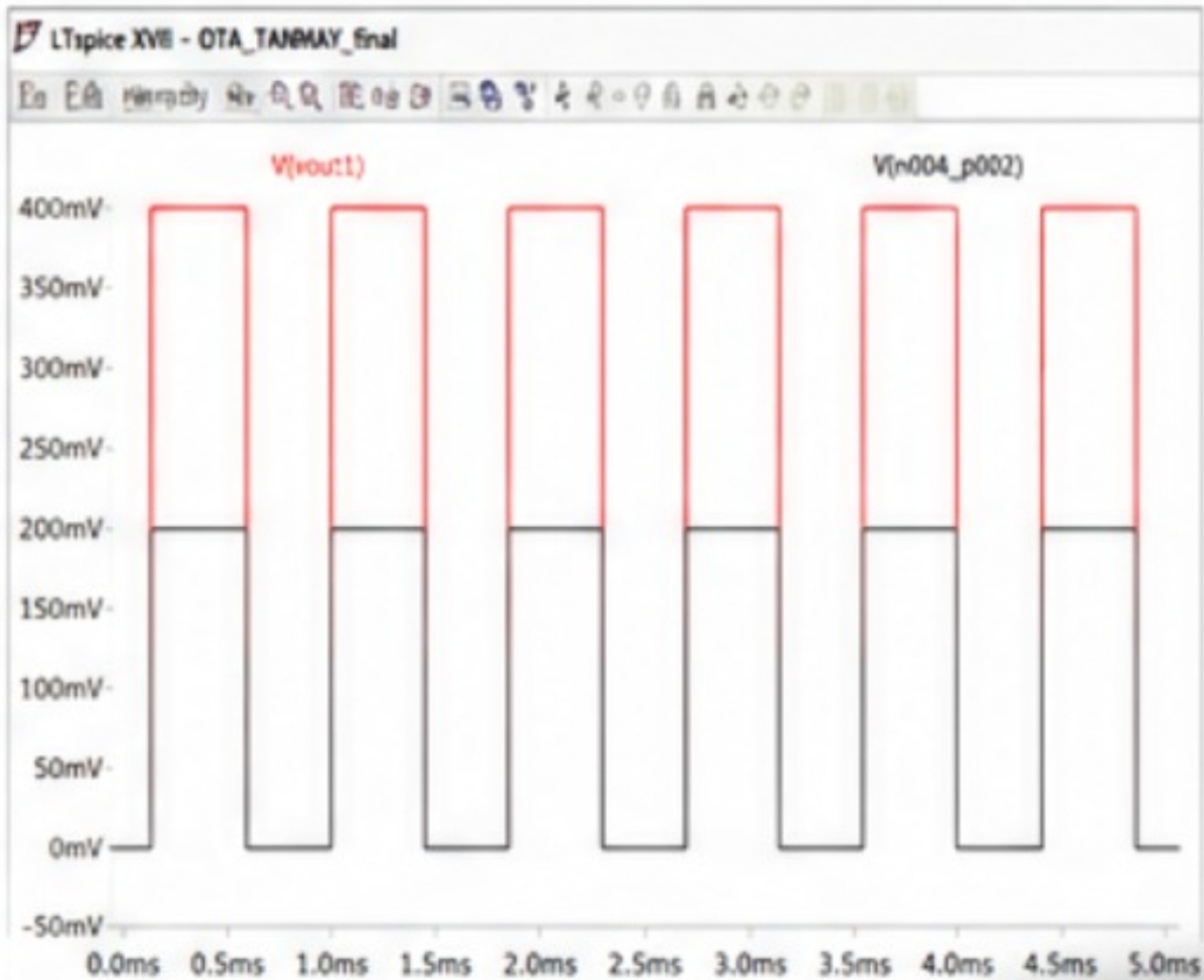


DC Gain

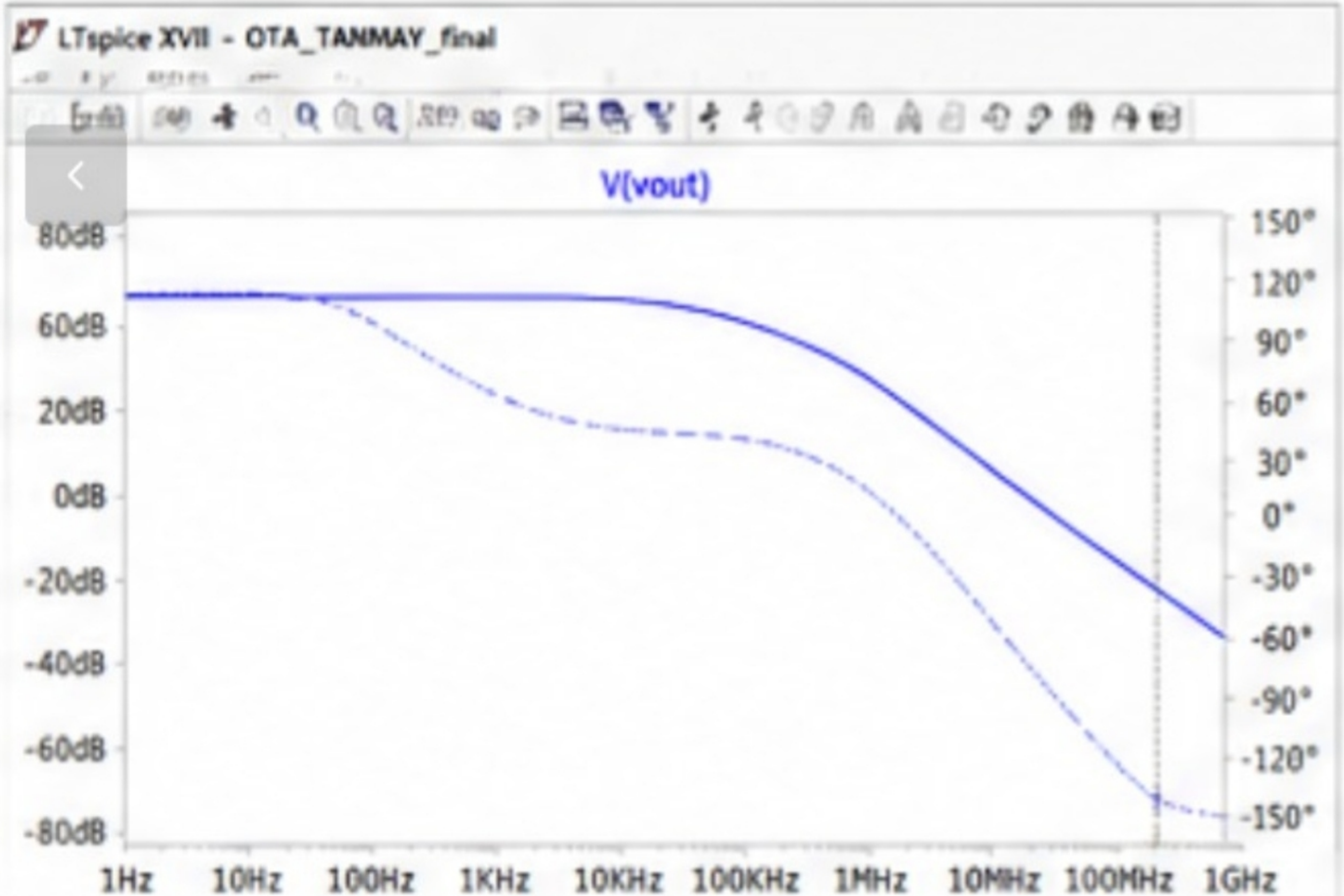


DC Gain

Blue : Stage 1 DC Gain


Black : Net DC Gain

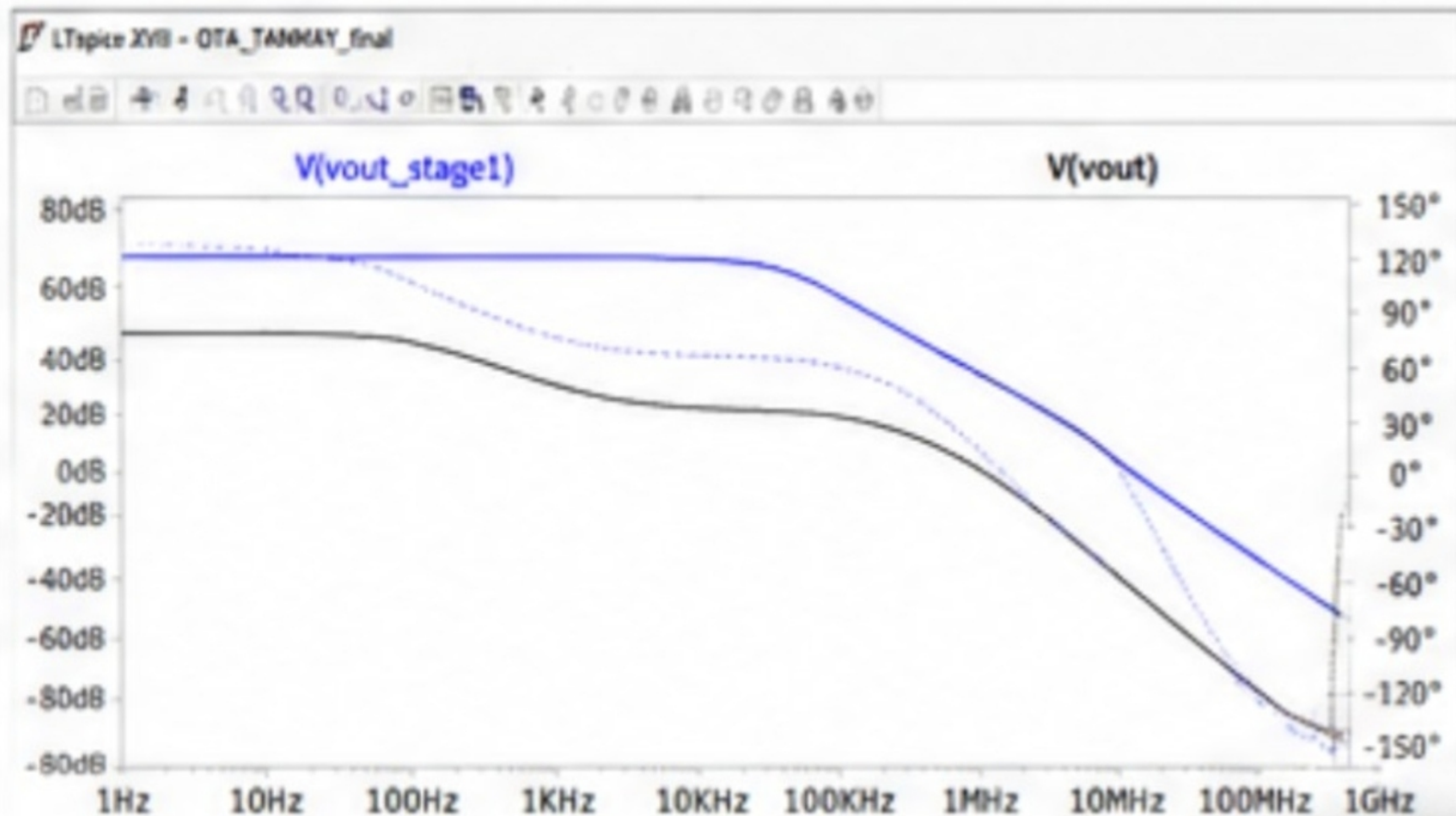

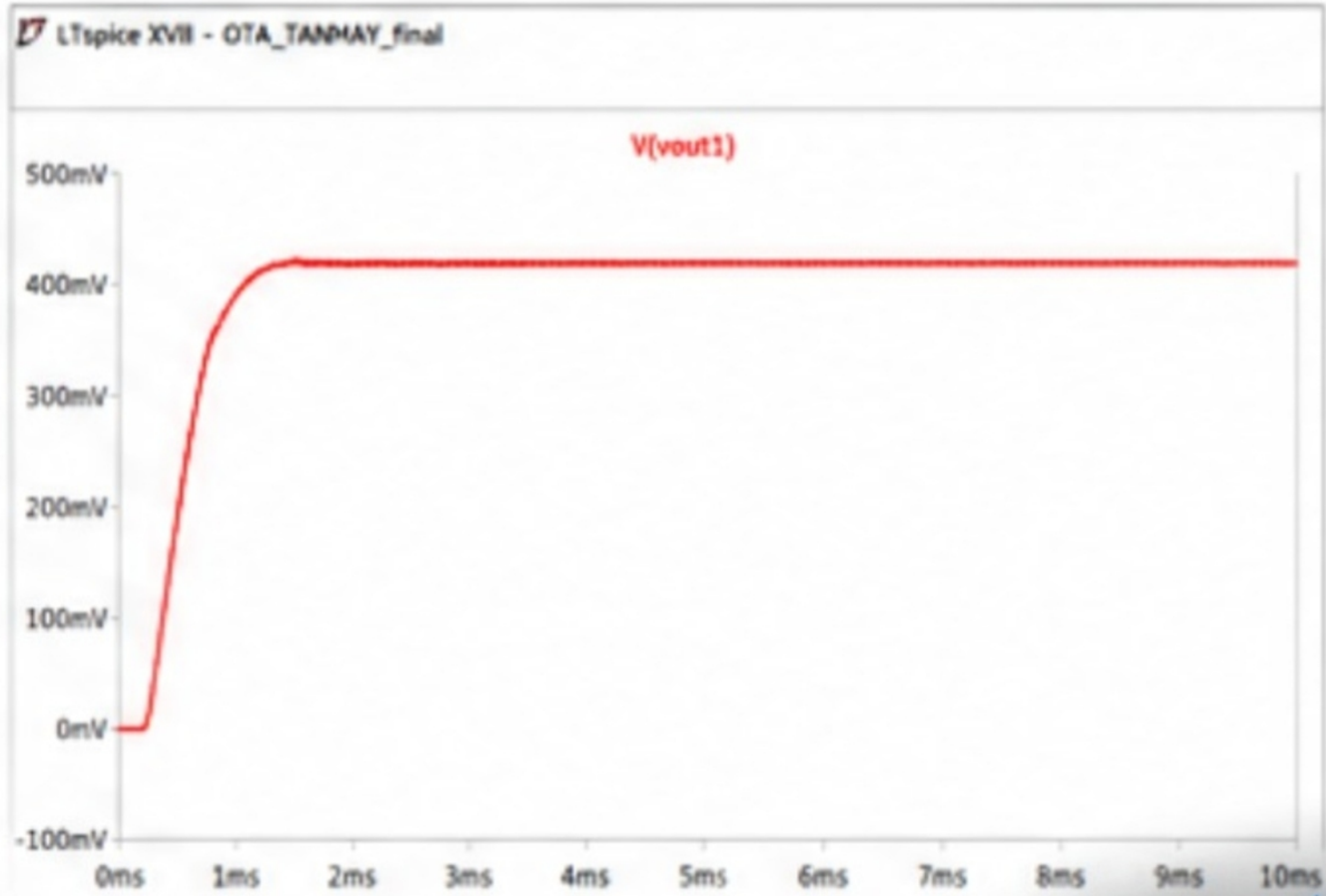
Transient Response of Closed loop amplifier with step input 0.2V



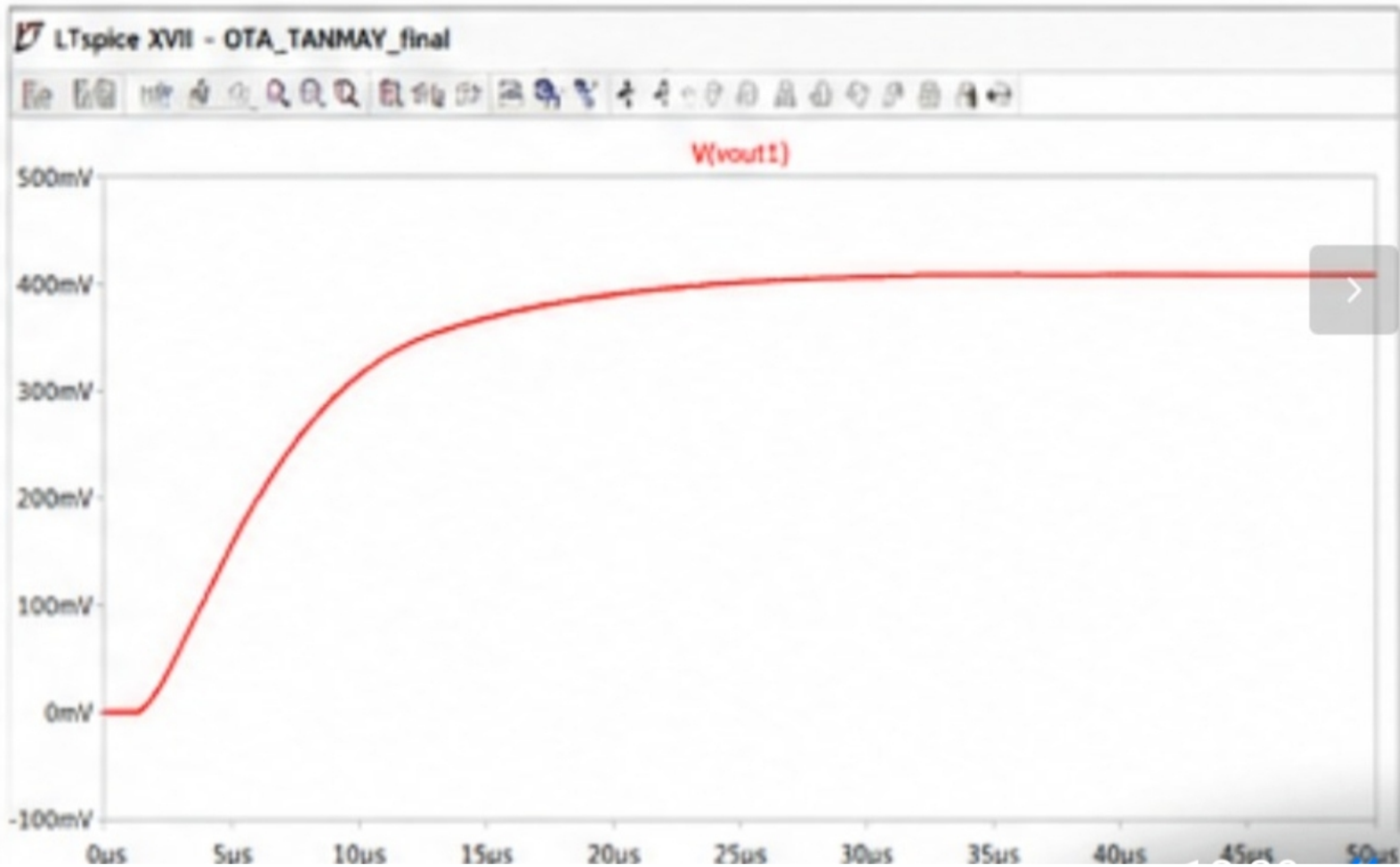Transient Response of Closed loop amplifier with step input 0.2V



Phase Margin

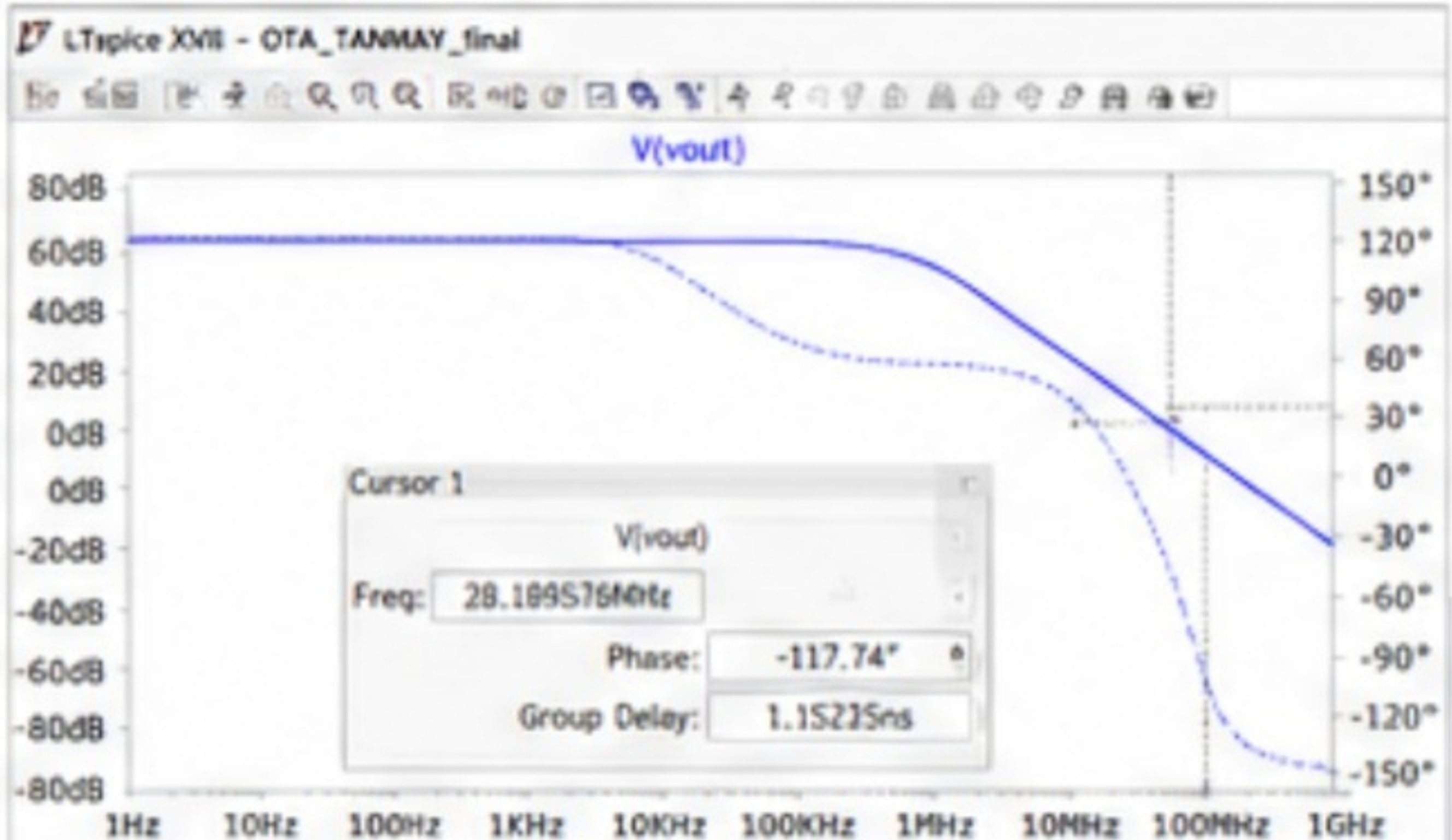

Phase margin :

$$180 - 117.74 = 62.26$$

DC operating points

LTspice XVII - OTA_TAMMAY_final



--- Operating Point ---

			Id(M0):	1.500000μ	device_current
			Id(M1):	1.500000μ	device_current
V(vdd):	1.80000	voltage	Id(M2):	750.00009n	device_current
V(vdiff):	899.99787m	voltage	Id(M3):	750.00009n	device_current
V(vout):	400.00021m	voltage	Id(M4):	1.500000μ	device_current
V(vout1):	399.99958m	voltage	Id(M5):	750.00009n	device_current
V(n004):	1.09999998	voltage	Id(M6):	750.00009n	device_current
V(n004_p002):	200.00002m	voltage	Id(M7):	1.500000μ	device_current

DC operating points

LTspice XVII - OTA_TANMAY_final



I(I1):	3.000000μ	device_current	V2#branch:	90.000000μ	current
I(V1):	-3.000000μ	device_current	V3#branch:	-1.500000μ	current
I(V2):	90.000000μ	device_current	I(C1):	-22.611508p	device_current
I(V3):	-1.500000μ	device_current	I(C2):	-570.45126p	device_current
			I(C3):	-2.2611508n	device_current